

## TUTORIAL 3: Logic Gates Overview

1. For a 2-input NOR gate functioning as a negative-AND gate, output X is HIGH if both inputs A and B are HIGH.

FALSE       $A=1$     $AB=1$   
                   $B=1$     $\overline{AB}=0$  (LOW)      TRUE / FALSE

2. A two-input XNOR gate will produce a HIGH output when both inputs are equal.

TRUE       $X=A \odot B$        $A=0, B=0$        $A=1, B=1$   
                   $=AB + \overline{A}\overline{B}$        $X=0+1=1$  (HIGH)       $X=1+0=1$  (HIGH)      TRUE / FALSE

3. A NOR gate with inverters at the inputs has the same logic function as an AND gate.

TRUE      NOR gate,  $X=\overline{A+B}$        $\overline{\overline{A}\overline{B}} = A \cdot B$  (De Morgan's)  
                  with inverter,  $X=\overline{\overline{A+B}}$       = AND gate      TRUE / FALSE

4. A 2-input NAND gate and a 2-input NOR gate produces the same output when both inputs are HIGH.

TRUE      NAND      NOR  
                   $A$   $B$   $X$        $A$   $B$   $X$   
                  1 1 0      1 1 0      TRUE / FALSE

5. The \_\_\_\_\_ gate produces a HIGH output when all inputs are LOW.

a. NOR       $A$     $B$     $X$   
                  0   0   1  
   b. NAND      0   0   1  
                  0   0   0  
                  0   0   0  
                  0   0   0

6. A 2-input logic gate X produces a HIGH output when input A is LOW and input B is HIGH. Which of the following is NOT logic gate X?

a. OR       $A$     $B$     $X$   
                  0   1   1  
   b. NOR      0   1   0 (LOW)  
                  0   1   1  
                  0   1   1  
                  0   1   1

7. Complete the following questions:

- i) Draw the logic symbol of an XOR gate.
- ii) Give appropriate labels to the inputs and output.
- iii) Write its truth table.


i) XOR



iii)

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0


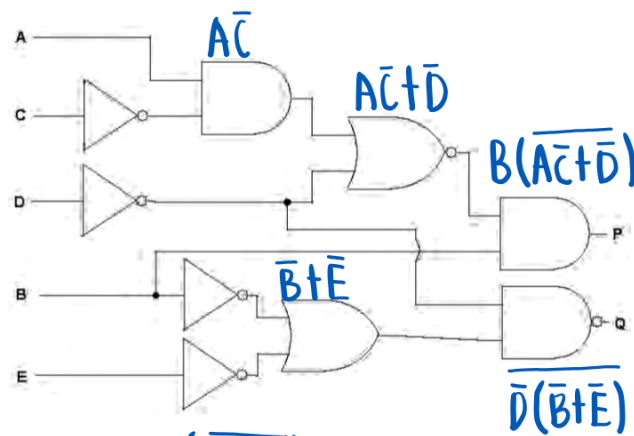
8. Write the Boolean expressions of output P and Q.



P = ?  $P = B(\bar{A}\bar{C} + \bar{D})$

Q = ?  $Q = \bar{D}(\bar{B} + \bar{E})$

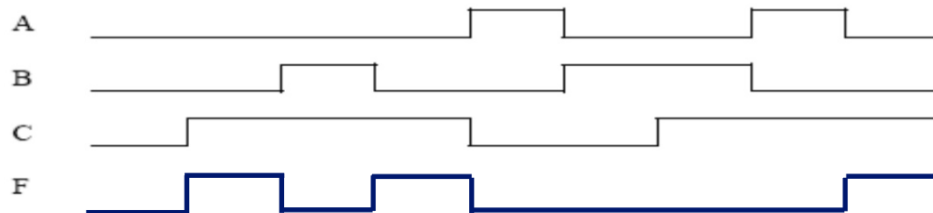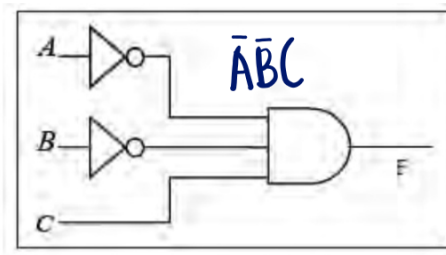
9. Complete the timing diagram based on the given input for the following logic diagram.



10. Draw symbol for the following gates:


i) 2-input AND gate

i)

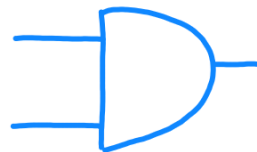

ii) 2-input OR gate

ii)

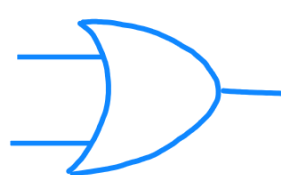


iii) Inverter

iii)




iv) 2-input NAND gate

iv)

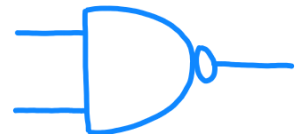

v) 2-input NOR gate

v)

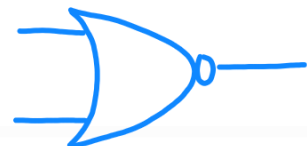

11. Given an AND gate with 3 inputs, what should the input values be to get an output of 1 (HIGH)?

All inputs are 1 (HIGH)

12. Given an OR gate with 3 inputs, what should the input values be to get an output of 1 (HIGH)?


At least one input is 1 (HIGH)

13. Fill in the table below, follow the example given.

Gate	Input			Output
	A	B	C	
AND	1	0	1	$X = 1 + 0 + 1 = 0$
OR	0	1	0	$X = 0 + 1 + 0 = 1$
AND	1	1	1	$X = 1 + 1 + 1 = 1$
OR	0	0	0	$X = A + B + C = 0 + 0 + 0 = 0$
NOR	1	1	1	$X = 1 + 1 + 1 = 0$
AND	1	0	0	$X = 1 + 0 + 0 = 0$

14. Given the input waveform(s) below, show the appropriate output waveform,  $X$ , with a timing diagram.

- i) XNOR
- ii) XOR
- iii) NAND

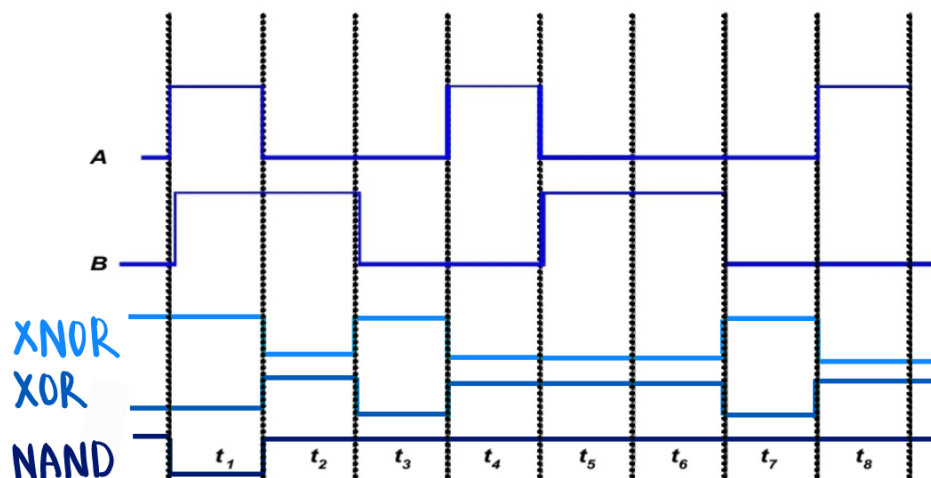

15. Identify the following devices according to logic function:

- i) 74LS04 Hex Inverter.
- ii) 74ALS10 Triple 3-input NAND Gate.
- iii) 74HC00 Quad 2-input NAND Gate.

16. Given the logic gates below, write the logic expression for it.

- i)  $T = XYZ$
- ii)  $T = X + Y + Z$
- iii)  $W = \overline{\overline{X}} = X$

