

BACKGROUND

Our project focuses on a Network Packet Transmission Monitoring System based on combinational and sequential circuits. This system allows users to select data sources and destinations while ensuring efficient routing and rule compliance.

COMBINATIONAL CIRCUIT COMPONENTS:

- Basic Gates: AND, OR, NOT
- Input Switches
- 1-bit Output Display
- 4-bit Hex Input
- 4-bit Comparator
- 8x1 Multiplexer
- 1x8 Demultiplexer

SEQUENTIAL CIRCUIT COMPONENTS:

- T Flip-Flop
- Clock Generator

EXTRA FEATURES:

- Fun Concept Display
- Error Detection
- Password system



PROBLEM STATEMENT

INEFFICIENT ROUTING

UNAUTHORIZED DATA ACCESS

LACK OF REAL-TIME MONITORING CAPABILLITIES

SUGGESTED SOLUTION



- Issue: inefficient routing
- Solution: implemented a 1-of-8

 Multiplexer and 1-to-8 Demultiplexer

 along with 3-bit selector to ensure the

 data can successfully transmitted to

 desired destination.

3

- Issue: lack of real-time monitoring capabilities
- Solution: comparator and clock enabler which allow users to control when to transmit the data and monitor the data through screen.

2

- Issue: unauthorized data access
- Solution: password protected system ensuring that only authorized personnel can set the maximum number of packets for transmission. Users need to input the correct password to enable the clock and store and transmit the data.



- Extra feature: error detection system
- Allows users to identify and fix the issues quicker, enhancing the efficiency of troubleshooting the circuit.

REQUIREMENTS

01.

Input switch

- allow the user to switch on or switch off the input computer and output computer.
- control the status (O or 1) of PRE_bar and CLR_bar

02.

<u>Multiplexer</u>

• 1-of-8 multiplexers are used to **select 1 computer out of 6 computers** as the data source.

03.

Demultiplexer

• 1-to-8 demultiplexers are used to route the data from the input computer to 1 computer out of 6 computers as the output computer.

04.

Clock Enabler

- control the synchronization clock pulse between the input and output computers.
- By toggling the clock enabler, users can enable and disable the clock

05.

4-bit input DIP switch

- consists of **four individual switches packaged together**, with each switch capable of being toggled on or off independently
- used as selector to select the input computer and output computer.
- Users can set the DIP switches according to **Rules 1** to address the input data to the desired output computer accurately.

06.

Comparator

- compare two sets of data
- provide an output indicating whether the input values are equal, greater, or smaller.

07.

3-bit count-up Counter

• designed to increase the count value by one with each clock pulse. The 3 output lines allow it to count from 0 to 7 in binary (000 to 111).





REQUIREMENTS

08.

Error detector

- 8-bit output LED Array that detects error through the status of each single LED.
- When a certain light doesn't light up, it indicates that there exists error in that part
- allows users to **quickly identify** and **troubleshoot** system faults for efficient maintenance.

09.

8-bit output LED array

 consists of eight LEDs that display the binary output of the system. Each LED represents a single bit, turned on indicates value '1' and turned off indicates value '0.'

10.

Password system

- ensure security and control access to the system.
- Users must input a valid hexadecimal code to unlock it. If the input password matches, the system grants access; otherwise, it remains locked.

11.

Input One Hex

- allows user to enter a hexadecimal value as input
- simplifies data entry by converting user-friendly hex inputs into binary data.

12.

PRE_bar

- set the output to high
- when PRE_bar is set to 0, the seven-segment display will show the highest number of packets stored.

13.

CLR_bar

- clear the output and set it to low (O)
- when CLR_bar is set to 0, the seven-segment display will show 0.

 
14.

7-segment display

• A 7-segment display is an electronic device that shows numerical digits and some characters. It's made up of seven LED segments that are arranged in a specific pattern.








MUX AND DEMUX

 
- Both consist of 6 computers
- 2 MUX and 2 DEMUX
- Transmitting data between Lab A and Lab B




INPUT

- DATA A1 Clock signal
- ON A1 Power on switch
- When ON A1 is 1 (HIGH) turned on
- When ON A1 is 0 (LOW) turned down
- Connected 2-input AND gate

OUTPUT

 


 - ON B6 Power on switch
- When ON B6 is 1 (HIGH) turned on
- When ON B6 is 0 (LOW) turned down
- ON B6 and output Q are connected to 2-input AND gate




3-BIT SYNCHRONOUS T FLIP-FLOP COUNTER

 - JK Flip-Flop used to imitate T Flip-Flop
- J=K=1
- 2 states (toggle & no change)
- Flip-Flop only work if clock input is




COMPARATOR

 - 4 inputs (A0-A3) 4-bit HEX input
- Other 3 inputs each output of Flip-Flop




ERROR DETECTION

 - First light doesn't light up: issue in comparator
- Second light doesn't light up: issue in password
- Third light doesn't lit: issue in TRX_Clk
- Fourth light doesn't light up: issue in PowerTRX
- Fifth light doesn't light up: issue in source and destination




CLOCK ENABLER

 - 5-input AND gate
- 1st input : from OR gates that combines all computers
- 2nd input : from PowerTRX
- 3rd input : from TRX clock
- 4th input : from password system
- 5th input: from comparator



PASSWORD SYSTEM

 
- Built using logic gates
- Take input from four sevensegment display
- Checks if the entered password matches 4E8D (hexadecimal).
- NOT gates invert certain bits.
- AND gates verify each digit's correctness.
- A final AND gate combines results.
- Output at error detector = 1 (HIGH)
 if the password matches.



FUN DISPLAY

  The fun concept display is built using a 1x2 DEMUX, clock generator, switches and the LEDs as the output. This fun concept display with the title "GROUP 7" was built to make the deeds circuit more appealing.





- simple and user friendly design
- input switches, seven-segment displays, LEDs, an LED array for outputs, a 4-bit comparator, a 3-bit up counter, a multiplexer and demultiplexer, a clock, and basic logic gates.
- to enchance security: integrated passwordprotected system connected to counter – using 3 bit T flip flop
- ensures incorrect data is not stored when an invalid password is entered
- error detection feature: enables users identify and resolve issues



Challenges and Solutions

- ensuring accurate packet routing and implementing secure password system - continuous debugging and teamwork
- lack of familiarity with Deeds software – further explore and study more

Future Prospects

- depend on understanding of circuit optimization, data security, digital design
- develop more advanced circuit with additional features
- enhancing our skills
- apply to real-world applications

Strentghs and Areas for Improvement

- Shee Tong main designer
- other team member also contribute to project report and presentation slides
- work together key role
- system only supports a maximum of 8 information packets (3 bit ff)
- implement additional flip-flop





Thank you very much!